

Registration No.:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

B.Tech/IDD  
EEPC2001

3<sup>rd</sup> Semester Regular Examination: 2024-25

Electrical Circuit Analysis

ELECTRICAL & C.E, ELECTRICAL, EE, EEE, ETC, ECE, ECE, AEIE, EEVDT

Time: 3 Hours

Max Marks: 100

Q.Code: R565

Answer Question No.1 (Part-I) which is compulsory, any eight from Part-II and any two from Part-III.


The figures in the right-hand margin indicate marks.

Part-I

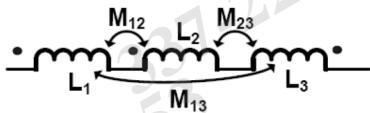Q1 Answer the following questions:

(2 x 10)

- State the order of the mentioned matrices (I) Reduced incidence matrix (II) complete incidence matrix (III) Tie set matrix (IV) Cut set matrix.
- State and explain Millman's theorem giving an example.
- State the condition of reciprocity and symmetry of ABCD parameters.
- Draw T- and  $\pi$ - networks and write the z and y parameters in terms of its side and middle arm impedances respectively.
- Write the expressions of selectivity, bandwidth, and Q factor in a series RLC circuit.
- Find the Laplace inverse of  $\frac{2s}{(s+1)^2}$ .
- The current in the inductor is given by  $i(t) = \frac{1}{L} \int_0^t v(t) dt + i(0)^+$   
What is the equivalent circuit in s-domain?
- Draw a first order active filter. Briefly explain its characteristics.



- Find the equivalent inductance in figure above.
- What are the necessary and sufficient conditions for a rational function  $F(s) = P(s)/Q(s)$  to be a positive real function?

Part-II

Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve)

(6 x 8)

- Explain the significance of cutset matrix with a suitable example.
- State and explain Reciprocity theorem with a suitable example.
- Using Millman's theorem, find the voltage across  $10\Omega$  resistor as shown in Fig.1.
- Write the loop equations in matrix form for the given network in Fig.2.
- Derive the open circuit voltage ratio  $V_2(s)/V_1(s)$  for the circuit shown in Fig.3. Draw its pole-zero plot.

- f) A resistance of  $4\Omega$  and an inductance of  $0.1\text{H}$  are connected in series and excited by a voltage  $v = 100\sin 40t$ . Find an expression for the current. The initial current in the circuit is zero.

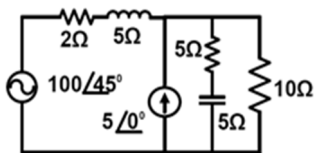


Fig.1

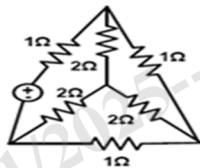


Fig.2

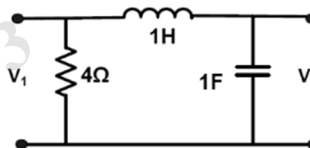


Fig.3


- g) For a series R-L-C circuit, show that  $\omega_0^2 = \omega_1 \cdot \omega_2$ , where  $\omega_0$ ,  $\omega_1$  and  $\omega_2$  have their usual meanings.
- h) Find the expression for current in a series R-C circuit with a rectangular pulse of width 'T' and magnitude 'E' using Laplace Transform. Assume zero initial condition for the capacitor.
- i) Find the expression for current in a series R-L-C circuit with a DC voltage of  $10\text{V}$ , the values of the elements are  $2\Omega$ ,  $1\text{H}$ , and  $\frac{1}{2}\text{F}$  respectively. Assume zero initial condition.
- j) Explain the terms Self-inductance, Mutual Inductance, and Coefficient of coupling. Establish the relation of the above terms.
- k) Test the polynomial  $Q(s) = s^8 + 3s^7 + 10s^6 + 24s^5 + 35s^4 + 57s^3 + 50s^2 + 36s + 24$  for its Hurwitz character.
- l) A function is given as  $F(s) = \frac{(s^2+1)(s^2+16)}{s(s^2+4)}$ . Realize it in the Foster-I form.

### Part-III

#### Only Long Answer Type Questions (Answer Any Two out of Four)

- Q3 a) State and prove Maximum Power Theorem. Describe all the three cases. (10)

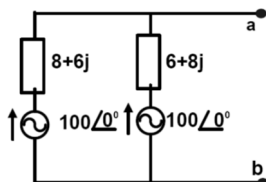- b) Determine the maximum power in a load resistor connected across the terminals a, b of the network shown above. (6)



terminals a, b of the network shown above.

- Q4 a) The response of a network to an impulse function is given by  $0.25(e^{-0.5t} - e^{-2.5t})$ . Determine the response of the network to a step function. (8)

- b) By applying Laplace Transform method derive the expressions for transient current (at  $t = 0+$ ) in case of (i) a series R-L circuit and (ii) a series R-C circuit by assuming zero initial conditions and a sudden switching of the networks to a step input at  $t = 0$ . (8)

- Q5 a) Deduce the expression for z- parameters in terms of h-parameters for a 2-port network and vice versa. (8)

- b) Two 2-port networks-1 and 2 have ABCD parameters  $A_1 = 1.5$ ,  $B_1 = 11\Omega$ ,  $C_1 = 0.25$  siemens and  $D_1 = 2.5$  for network-1 and  $A_2 = 5/3$ ,  $B_2 = 4\Omega$ ,  $C_2 = 1$  siemens and  $D_2 = 3$  for network-2. If two networks are connected in parallel, obtain the admittance parameters of the resulting network. (8)

- Q6 a) Test the function for positive realness. (6)

$$Z(s) = \frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$$

- b) Obtain the Cauer forms for the function. (10)

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$$