

Registration No.:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

B.Tech  
REE3C002

3<sup>rd</sup> Semester Back Examination: 2024-25

NETWORK THEORY

BRANCH(S): AEIE, EEE, EIE, ELECTRICAL, ELECTRICAL & C.E.

Time: 3 Hours

Max Marks: 100


Q.Code: R577

Answer Question No.1 (Part-I) which is compulsory, any eight from Part-II and any two from Part-III.

The figures in the right hand margin indicate marks.

Part-I

Q1 Answer the following questions: (2 x 10)

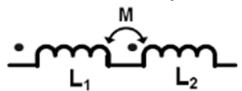- State Substitution Theorem with an example.
- State Thevenin's theorem for a circuit containing sinusoidal ac sources.
- Explain the significance of dot convention in electric circuits.
- The Z-parameters of a two-port network are given as  $Z_{11} = 5\Omega$ ,  $Z_{22} = 7\Omega$ ,  $Z_{12} = Z_{21} = 3\Omega$ . Draw its T-equivalent circuit.
- Represent a common emitter (CE) transistor as a 2-port network using h-parameters.
- Define an Impulse function and write its Laplace Transform.
-  Find the equivalent inductance in the figure given above.
- Find the complex power, when the given voltage is  $125 + 30j$  Volt and current is  $25 + 12j$  Amp.
- Differentiate between series and parallel resonance.
- Write the conditions for symmetry for a 2-port network in z, y, h, and ABCD parameters.

Part-II

Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)

- State and explain Reciprocity theorem with an example.
- What is 'Duality' in electrical networks? Explain with suitable examples.
- Find the equivalent inductance of the set up as shown in Fig.5.
- The Z-parameters of a two-port network are given as  $Z_{11} = (2s + 1/s)$ ,  $Z_{12} = Z_{21} = 2s$ ,  $Z_{22} = (2s + 4)$ . Find the T-equivalent of the network.
- For a series R-L-C circuit, show that  $\omega_0^2 = \omega_1 \cdot \omega_2$ , where  $\omega_0$ ,  $\omega_1$ , and  $\omega_2$  have their usual meanings.
- For an initially relaxed series RC circuit, derive the expression for the charging current through it for a unit step excitation.
- Find the initial and final value of the function f(t), whose Laplace Transform is given as 
$$F(s) = \frac{(s+4)}{(s+1)(s+3)}$$
- Write short notes on the various types of interconnections possible in two-port networks.

- i) Find the expression for current in a series R-C circuit with a rectangular pulse of width 'T' and magnitude 'E' using Laplace Transform. Assume zero initial condition for the capacitor.
- j) Explain the terms Self-inductance, Mutual Inductance, and Coefficient of coupling. Establish the relation of the above terms.
- k) Derive the expression for average power over a time period (T) where  $v(t) = V_m \sin(\omega t + \beta)$  and  $i(t) = I_m \sin(\omega t + \alpha)$ .
- l) Describe the various types of responses in a series R-L-C circuit with a step input.

**Part-III**

**Only Long Answer Type Questions (Answer Any Two out of Four)**

- Q3** (a) State and explain (all three cases) Maximum Power Transfer Theorem. (10)
- (b) Calculate the value of the load resistance  $R_L$ , that would draw maximum power from the rest of the circuit as shown in Fig.1. (6)

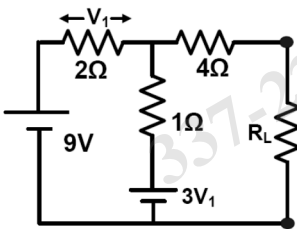


Fig.1

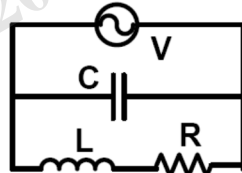


Fig.2

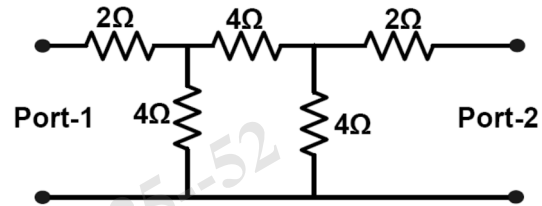


Fig.3

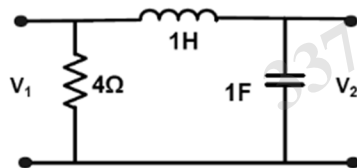


Fig.4

Fig.5

- Q4** (a) Derive the relationship for bandwidth, cut-off frequencies and Quality factor for a series RLC circuit. (10)
- (b) Find the frequency of resonance for the following parallel resonance circuit in Fig.2 (6)
- Q5** (a) By applying Laplace Transform method derive the expressions for transient current (at  $t = 0+$ ) in case of (i) a series R-L circuit and (ii) a series R-C circuit by assuming zero initial conditions and a sudden switching of the networks to a step input at  $t = 0$ . (10)
- (b) A resistance of  $4\Omega$  and an inductance of  $0.1H$  are connected in series and excited by a voltage  $v = 100\sin 40t$ . Find an expression for the current. The initial current in the circuit is zero. (6)
- Q6** (a) Calculate the transmission or ABCD parameters for the two port network shown in Fig.3. Hence find out the impedance parameters by applying the conversion technique. (10)
- (b) Derive the open circuit voltage ratio  $V_2(s)/V_1(s)$  for the circuit shown in Fig.4. Draw its pole-zero plot. (6)